

CSC 411


Computer Organization (Spring 2024)
Lecture 21: Sequential logic

Prof. Marco Alvarez, University of Rhode Island

Disclaimer


Some figures and slides are adapted from:

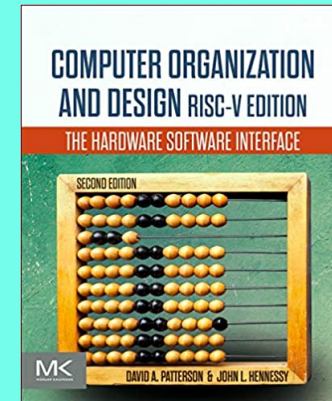Computer Organization and Design (Patterson and Hennessy)
The Hardware/Software Interface




Storing 1 bit


Storing 1 bit

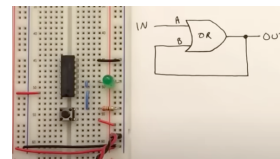

$0 \Rightarrow 0$

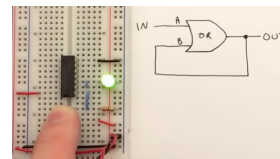

$1 \Rightarrow 1$

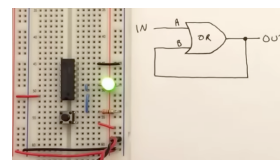

$0 \Rightarrow 1$


remembers past value,
but can't reset it

<https://www.youtube.com/watch?v=KM0DdEaY5sY>

Storing 1 bit

Two stable states

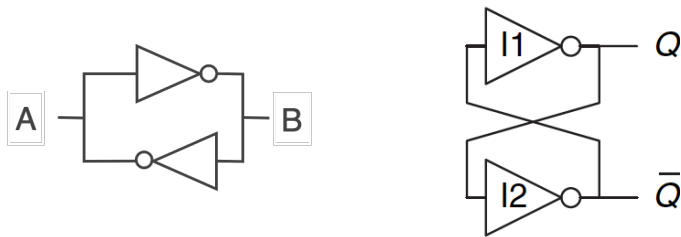- third possible metastable with inputs oscillating between 0 and 1



Not useful without a mechanism for changing the output (Q)


SR-latch

Set-reset latch

- when S is high output 1, when R is high output 0, when both are low preserve the current state (memory!)
- use a pair of cross-coupled NOR gates (could also use NAND gates)

R	S	Q	
0	0	Q	HOLD
0	1	1	SET
1	0	0	RESET
1	1	INVALID	

breaks the invariant

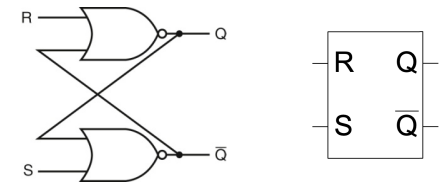


Invariant: always two outputs Q and \bar{Q}

D-latch (level triggered)

Guarantees correct operation


- adds an inverter to avoid the undef state (S=1 R=1)
- Clock signal C (clock) controls when to store D
- when C is high, Q continuously changes as D changes (**transparent mode**) — latching
- when C is low, maintain current state, Q doesn't change with D (**opaque/latch mode**)

C	D	Q	
0	0	Q	HOLD
0	1	Q	HOLD
1	0	0	RESET
1	1	1	SET

 

Practice

 
Consider the following operation of a D-latch



Note there is a propagation delay from D to Q

Draw the values of Q over time


- is there a problem with the output?

 

C	D	Q
0	0	Q
0	1	Q
1	0	0
1	1	1


D-flip-flop (edge triggered)

- D-latches are transparent
 - doesn't help if we want to ensure data is available during the **entire clock cycle**
- D-flip-flop with a **"falling"** edge trigger
 - **master** and **slave** latches connected in series
 - the flip-flop updates its stored value only on a falling clock edge
 - state updated in a synchronized fashion: when C rises $0 \rightarrow 1$, Q does not change; when C falls $1 \rightarrow 0$, Q changes


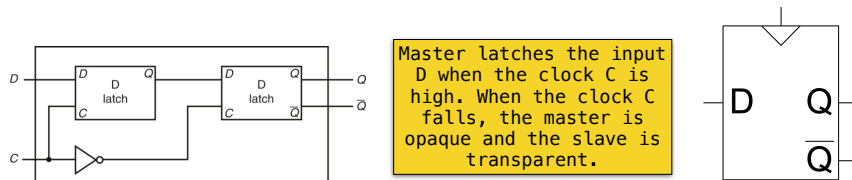


Practice

 - Consider the following operation of a D-flip-flop with a falling-edge trigger



- Draw the values of Q and X over time

  


D-latch vs D-flip-flop

- D-latch is a **transparent** storage element
 - the output follows the input as long as the clock signal is active
 - captures and propagates any **temporary glitches** or **fluctuations** on the input
- D-flip-flop is an **edge-triggered** storage element
 - on the clock edge (rising/falling depending on implementation), the D-flip-flop will latch the value on the D input
 - **output will remain constant until the next clock edge**, even if the D input changes in the meantime
 - d-flip-flops filter out temporary glitches or fluctuations on the input and therefore are useful when we want to capture and hold a stable value, rather than continuously track an input


Register file

Register

 - Can use D-flip-flops in parallel
 - shared clock, may have extra inputs, e.g., write
 - e.g., a 4-bit register needs 4 d-flip-flops




 Register, stores 4 bits and can be read from and written to




Register file

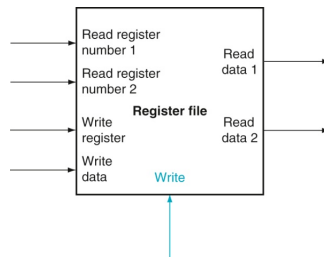- For RISC-V, the register file has two read ports and one write port
 - five inputs and two outputs
 - control input **Write** is shown in color
- Very fast storage with only a few gate delays




Read ports

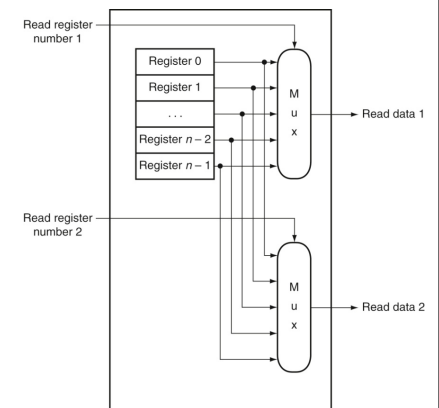- Two read ports for a register file with n registers
 - read ports use a pair of multiplexors, each 32 bits wide
 - register read number is used as the multiplexor selector signal
- In RISC-V, most instructions have two source operands




Write port

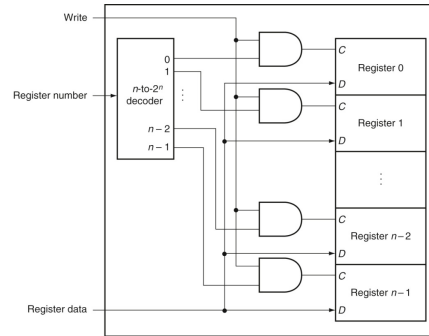- Implementation of the write port for a register file
 - requires a decoder and the write signal (clock) to generate the C input to the registers
- All three inputs have setup and hold-time constraints that ensure that the correct data are written into the register file



32-bit register file

 - A register file with 32 registers, each storing 32 bits



By using a rising edge triggered register, we can write and read in the same clock cycle